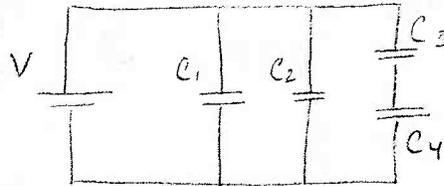


P #34a

Ch 16 - pg 526

$$\begin{aligned}w_1 \quad C_1 &= 4.0 \mu\text{F} = 4.0 \times 10^{-6} \text{ F} \\ C_2 &= 2.0 \mu\text{F} = 2.0 \times 10^{-6} \text{ F} \\ C_3 &= 24 \mu\text{F} = 24 \times 10^{-6} \text{ F} \\ C_4 &= 8.0 \mu\text{F} = 8.0 \times 10^{-6} \text{ F}\end{aligned}$$

$$V = 36 \text{ V}$$



Find  $C_{eq}$  for  $C_3$  and  $C_4$  in series

$$\frac{1}{C_{34}} = \frac{1}{C_3} + \frac{1}{C_4}$$

$$C_{34}^{-1} = 24 \mu\text{F}^{-1} + 8.0 \mu\text{F}^{-1}$$

$$C_{34} = 6.0 \mu\text{F}$$

Find  $C_{eq}$  for  $C_1$ ,  $C_2$ , and  $C_{34}$  in parallel

$$C_{eq} = C_1 + C_2 + C_{34}$$

$$= 4.0 \mu\text{F} + 2.0 \mu\text{F} + 6.0 \mu\text{F}$$

$$C_{eq} = 12.0 \mu\text{F}$$