

P # J

Ch 16 - Worksheet


$$C_1 = C_2 = C_3 = 2.0 \mu F$$

To increase C , use parallel circuits.

$$C_{eq} = C_1 + C_2 + C_3$$

$$= (2.0 \mu F) \cdot 3$$

$$C_{eq} = 6.0 \mu F$$

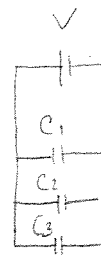


b) To decrease C , use series circuits

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_{eq}^{-1} = 3 \cdot (2.0 \mu F)^{-1}$$

$$C_{eq} = .666 \mu F$$

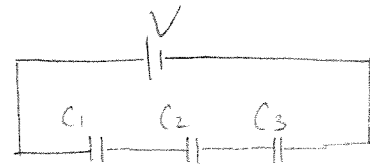

c) By trial & error, find a combination of series & parallel circuits

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{12}^{-1} = (2.0 \mu F)^{-1} + (2.0 \mu F)^{-1}$$

$$C_{12} = 1.0 \mu F$$

$$C_{eq} = C_{12} + C_3$$

$$= (1.0 \mu F) + (2.0 \mu F)$$

$$C_{eq} = 3.0 \mu F$$

