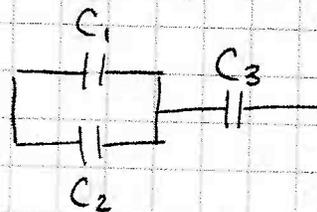


a) $C_1 = C_2 = C_3 = 100 \mu\text{F}$

For A:



$$C_{12} = \sum C_i \quad (C_1 \text{ and } C_2 \text{ are parallel})$$

$$= C_1 + C_2 = 100 \mu\text{F} + 100 \mu\text{F}$$


$$C_{12} = 200 \mu\text{F}$$

$$C_{eq}^{-1} = \sum C_i^{-1} \quad (C_{12} \text{ and } C_3 \text{ are series})$$

$$C_{eq}^{-1} = (200 \mu\text{F})^{-1} + (100 \mu\text{F})^{-1}$$

$$C_{eq} = 67 \mu\text{F}$$

b) For B:

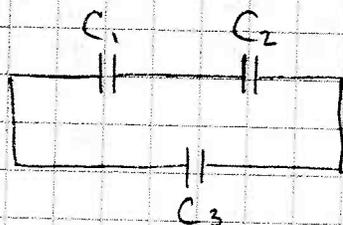

$$C_{12}^{-1} = \sum C_i^{-1} \quad (C_1 \text{ and } C_2 \text{ are series})$$

$$C_{12}^{-1} = (100 \mu\text{F})^{-1} + (100 \mu\text{F})^{-1}$$

$$C_{12} = 50 \mu\text{F}$$

$$C_{eq} = \sum C_i \quad (C_{12} \text{ and } C_3 \text{ are in parallel})$$

$$C_{eq} = 50 \mu\text{F} + 100 \mu\text{F}$$

$$C_{eq} = 150 \mu\text{F}$$