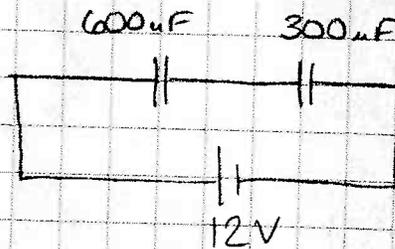


a) $C_1 = 600 \mu\text{F}$
 $C_2 = 300 \mu\text{F}$

$$V = 12.0 \text{ V}$$



$$C_{eq}^{-1} = \sum C_i^{-1} \quad (\text{series})$$

$$C_{eq}^{-1} = (600 \mu\text{F})^{-1} + (300 \mu\text{F})^{-1}$$

$$C_{eq} = 200 \mu\text{F}$$

b) $C_{eq} = 200 \mu\text{F}$
 $V_{eq} = 12 \text{ V}$

$$C_{eq} = \frac{Q_{eq}}{V_{eq}}$$

$$(200 \mu\text{F}) = \frac{Q_{eq}}{12 \text{ V}}$$

$$Q_{eq} = 2400 \mu\text{C}$$

For series: $Q_1 = Q_2 = Q_{eq}$ so

$$Q_1 = Q_2 = 2400 \mu\text{C}$$

c) $Q_1 = Q_2 = 2400 \mu\text{C}$
 $C_1 = 600 \mu\text{F}$
 $C_2 = 300 \mu\text{F}$

$$C_1 = \frac{Q_1}{V_1}$$

$$C_2 = \frac{Q_2}{V_2}$$

$$600 \mu\text{F} = \frac{2400 \mu\text{C}}{V_1}$$

$$300 \mu\text{F} = \frac{2400 \mu\text{C}}{V_2}$$

$$\boxed{V_1 = 4 \text{ V}}$$

$$\boxed{V_2 = 8 \text{ V}}$$