

$$\begin{aligned} \text{a) } R &= 100 \Omega \\ C &= 20.0 \times 10^{-6} \text{ F} \end{aligned}$$

$$\tau = R \cdot C$$

$$= (100 \Omega)(20.0 \times 10^{-6} \text{ F})$$

$$\tau = .002 \text{ sec}$$

$$\begin{aligned} \text{b) } V &= 9.0 \text{ V} \\ C &= 20.0 \times 10^{-6} \text{ F} \end{aligned}$$

$$C = \frac{Q}{V} \quad (20.0 \times 10^{-6} \text{ F}) = \frac{Q}{9 \text{ V}}$$

$$Q = 1.8 \times 10^{-4} \text{ C}$$

$$\text{c) } Q_{\text{max}} = 1.8 \times 10^{-4} \text{ C}$$

$$Q = (.632)(1.8 \times 10^{-4} \text{ C}) \quad (\text{63\% charged after 1 time constant})$$

$$Q = 1.14 \times 10^{-4} \text{ C}$$