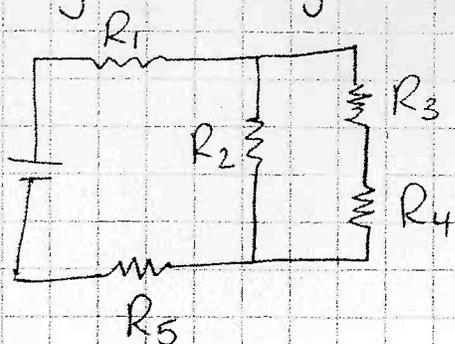


Redrawing the diagram...



$$\begin{aligned} R_1 &= 5\Omega \\ R_2 &= 5\Omega \\ R_3 &= 5\Omega \\ R_4 &= 5\Omega \\ R_5 &= 1.5\Omega \end{aligned}$$

Find R_{34} ...
(Series)

$$R_{34} = R_3 + R_4 = 5\Omega + 5\Omega$$

$$R_{34} = 10\Omega$$

Find R_{234} ...
(Parallel)

$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_{34}}$$

$$R_{234}^{-1} = (5\Omega)^{-1} + (10\Omega)^{-1}$$

$$R_{234}^{-1} = .3$$

$$R_{234} = 3.3\Omega$$

Find R_{eq} ...
(Series)

$$R_{eq} = R_1 + R_{234} + R_5$$

$$= 5\Omega + 3.3\Omega + 1.5\Omega$$

$$R_{eq} = 9.8\Omega$$