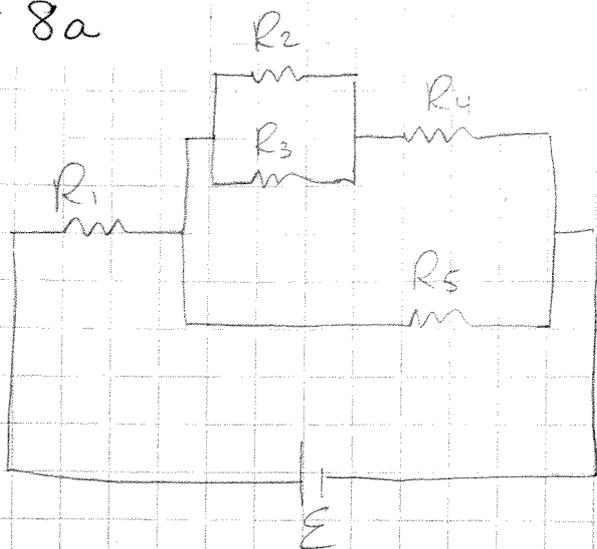


P # 8a

Ch 18 - pg 578

a)



$$R_1 = 3 \Omega$$

$$R_2 = 10 \Omega$$

$$R_3 = 5 \Omega$$

$$R_4 = 4 \Omega$$

$$R_5 = 3 \Omega$$

Find R_{23} ...
(Parallel)

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{23}^{-1} = (10 \Omega)^{-1} + (5 \Omega)^{-1}$$

$$R_{23}^{-1} = .3$$

$$R_{23} = 3.\bar{3} \Omega$$

Find R_{234} ...
(Series)

$$R_{234} = R_{23} + R_4$$

$$= 3.\bar{3} \Omega + 4 \Omega$$

$$R_{234} = 7.\bar{3} \Omega$$

Find R_{2345} ...
(Parallel)

$$\frac{1}{R_{2345}} = \frac{1}{R_{234}} + \frac{1}{R_5}$$

$$R_{2345}^{-1} = (7.\bar{3} \Omega)^{-1} + (3 \Omega)^{-1} = .47$$

$$R_{2345} = 2.1 \Omega$$

Find R_{eq} ...
(Series)

$$R_{eq} = R_1 + R_{2345}$$

$$= 3 \Omega + 2.1 \Omega$$

$$R_{eq} = 5.1 \Omega$$