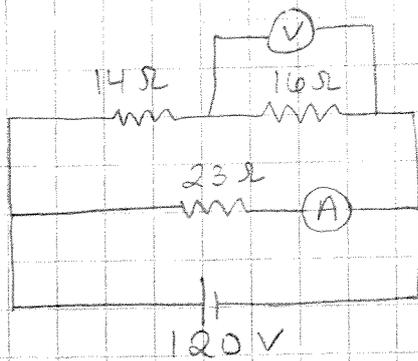


P # C

Ch 18 - Worksheet

a)



$$\begin{aligned} R_1 &= 23 \Omega \\ R_2 &= 14 \Omega \\ R_3 &= 16 \Omega \end{aligned}$$

b) $V_1 = V_{eq} = 120V$

$$R_1 = 23 \Omega$$

$$V_1 = I_1 \cdot R_1$$

$$(120V) = I_1 \cdot (23 \Omega)$$

$$I_1 = 5.2 A$$

c) $R_{23} = R_2 + R_3$
 $= (14 \Omega) + (16 \Omega)$
 $R_{23} = 30 \Omega$

$$V_{23} = V_{eq} = 120V$$

$$V_{23} = I_{23} \cdot R_{23}$$

$$(120V) = I_{23} \cdot (30 \Omega)$$

$$I_{23} = 4 A = I_2 = I_3$$

$$\begin{aligned} V_3 &= I_3 \cdot R_3 \\ &= (4A)(16 \Omega) \end{aligned}$$

$$V_3 = 64 V$$