

$$V = .6 \text{ V}$$

$$C = 200 \mu\text{F} = 200 \times 10^{-6} \text{ F}$$

$$R = 10 \Omega$$

a) S_1 is closed, so charge flows through R

$$V = I \cdot R$$
$$(.6 \text{ V}) = I \cdot (10 \Omega)$$

$$I = .6 \text{ A}$$

b) S_2 is open, so no charge flows to C

$$Q = \text{zero}$$

c) S_1 has not changed:

$$I = .6 \text{ A}$$

d) S_2 is closed, so charge flows to C

$$C = \frac{Q}{V} \quad (200 \times 10^{-6} \text{ F}) = \frac{Q}{.6 \text{ V}}$$

$$Q = .0012 \text{ C}$$