

$$C = 400 \mu\text{F}$$

$$R_1 = 20 \Omega$$

$$R_2 = 10 \Omega$$

$$V = 12 \text{ V}$$

a) Find R_{eq} :
(series)

$$R_{eq} = R_1 + R_2$$

$$= (20 \Omega) + (10 \Omega)$$

$$R_{eq} = 30 \Omega$$

Find I_1

$$V_{eq} = I_{eq} \cdot R_{eq}$$

$$12 \text{ V} = I_{eq} \cdot (30 \Omega)$$

$$I_{eq} = I_1 = .4 \text{ A}$$

b) Find V_2 :

$$V_2 = I_2 \cdot R_2$$

$$= (.4 \text{ A}) (10 \Omega)$$

$$V_2 = 4 \text{ V}$$

c) $V = V_2 = 4 \text{ V}$
 $C = 400 \mu\text{F}$

$$C = \frac{Q}{V} \quad \text{so} \quad 400 \mu\text{F} = \frac{Q}{4 \text{ V}}$$

$$Q = 1600 \mu\text{C}$$