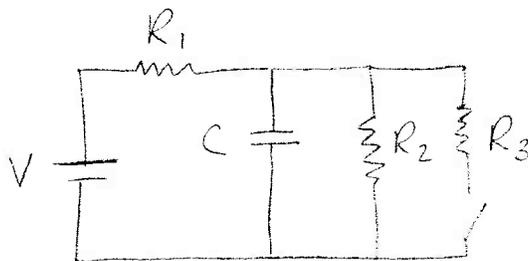


$$R_1 = R_2 = R_3 = 10 \Omega$$

$$C = 140 \mu\text{F}$$

$$V_{\text{eq}} = 12 \text{ V}$$



a) Find  $R_{23}$ :  
(Parallel)

$$R_{23}^{-1} = R_2^{-1} + R_3^{-1}$$

$$R_{23}^{-1} = (10 \Omega)^{-1} + (10 \Omega)^{-1}$$

$$R_{23} = 5 \Omega$$

Find  $R_{\text{eq}}$ :

$$R_{\text{eq}} = R_1 + R_{23}$$

$$= 10 \Omega + 5 \Omega$$

$$R_{\text{eq}} = 15 \Omega$$

Find  $I_{\text{eq}}$ :

$$V_{\text{eq}} = I_{\text{eq}} \cdot R_{\text{eq}}$$

$$12 \text{ V} = I_{\text{eq}} \cdot (15 \Omega)$$

$$I_{\text{eq}} = I_{23} = .8 \text{ A}$$

Find  $V_{23}$ :

$$V_{23} = I_{23} \cdot R_{23}$$

$$= (.8 \text{ A})(5 \Omega)$$

$$V_{23} = 4 \text{ V}$$

b)  $V_{23} = 4 \text{ V}$   
 $C = 140 \mu\text{F}$

$$C = \frac{Q}{V}$$

$$140 \mu\text{F} = \frac{Q}{4 \text{ V}}$$

$$Q = 560 \mu\text{C}$$